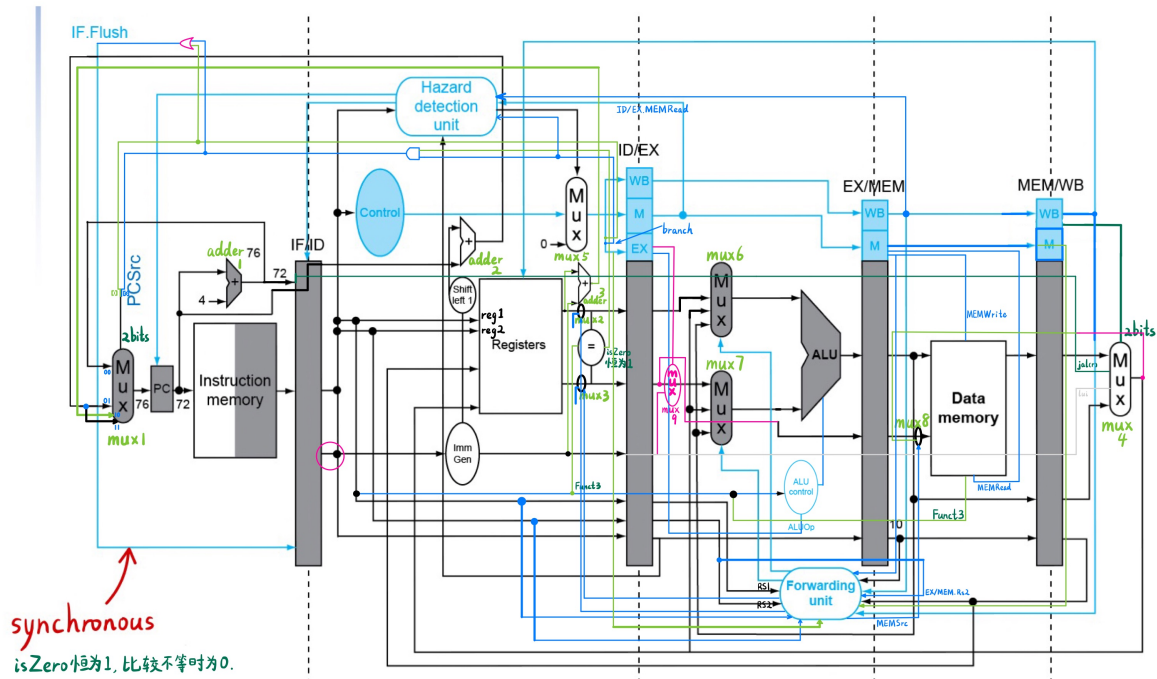


VE370 Lab 5 Report

Group 4 Wenqi Cao, Jingye Lin, Lan Wang

Modeling and Implementation

We modified the graph of pipelined processor to support hazard detection and fix. The new design is shown below:



Data and control hazards are solved by adding Hazard detection unit and Forwarding unit. The logic of judgement is shown below (some default conditions are emitted):

Hazard detection unit:

```
if (IDEX_MemRead && !ID_MemWrite) begin
    if (IDEX_RegRd == IFID_r1 || IDEX_RegRd == IFID_r2) begin
        // load-use
        PC_write=1'b0; IFID_write=1'b0; mux_con=1'b0; // insert nop
    end
    else // default
end
else if (ID_branch && IDEX_RegWrite) begin
    if ((IDEX_RegRd!=0) && (IFID_r1 == IDEX_RegRd || IFID_r2 == IDEX_RegRd))
    begin
        // R-branch
        PC_write=1'b0; IFID_write=1'b0; mux_con=1'b0;
    end
    else // default
end
else if (ID_branch && EXMEM_MemRead) begin
```

```

    if ((EXMEM_RegRd!=0) && (IFID_r1 == EXMEM_RegRd || IFID_r2 == EXMEM_RegRd))
begin
    // load-branch (two nops)
    // another nop is inserted by R-branch type
    PC_write=1'b0; IFID_write=1'b0; mux_con=1'b0;
end
else // default
end
else // default

```

Forwarding unit:

```

//ForwardingA (00: from register; 01: from MEM; 10: from EX)
//EX
if (EXMEM_RegWrite && (EXMEM_RegRd!=0) && EXMEM_RegRd == IDEX_r1 &&
!EXMEM_MemRead && !IDEX_MemRead && !IDEX_MemWrite)
    Forwarding_A = 2'b10;
//MEM
else if (MEMWB_RegWrite && (MEMWB_RegRd!=0) && MEMWB_RegRd == IDEX_r1)
    Forwarding_A = 2'b01;
else
    Forwarding_A = 2'b00;

//ForwardingB (00: from register; 01: from MEM; 10: from EX)
//EX
if (EXMEM_RegWrite && (EXMEM_RegRd!=0) && EXMEM_RegRd == IDEX_r2 &&
!EXMEM_MemRead && !IDEX_MemRead && !IDEX_MemWrite)
    Forwarding_B = 2'b10;
//MEM
else if (MEMWB_RegWrite && (MEMWB_RegRd!=0) && MEMWB_RegRd == IDEX_r2)
    Forwarding_B = 2'b01;
else
    Forwarding_B = 2'b00;

//Memsrsc (for the mux before writeData of memory)
if (MEMWB_RegRd == EXMEM_r2 && EXMEM_MemWrite)
    MemSrc = 1'b1;
else
    MemSrc = 1'b0;

//ForwardingEq (the selection signal of the mux of inputs for comparator)
if (EXMEM_RegWrite && (EXMEM_RegRd!=0) && EXMEM_RegRd == IFID_r1 &&
IFID_branch)
    Forwarding_Eq1 = 1'b1;
else
    Forwarding_Eq1 = 1'b0;

if (EXMEM_RegWrite && (EXMEM_RegRd!=0) && EXMEM_RegRd == IFID_r2 &&
IFID_branch)
    Forwarding_Eq2 = 1'b1;
else
    Forwarding_Eq2 = 1'b0;

```

Simulation Result


Hazard 1

```
00002e03  lw x28 0 x0
01c29c63  bne x5 x28 24 <wrong_branch>
01c283b3  add x7 x5 x28
```

instruction: 01c283b3 add x7 x5 x28

hazard type: a data hazard by load

resolve: use the hazard detection unit to add bubbles in it: PC_write=0, IFID_write=0, mux_con=0 for two clock cycles, and use forwarding unit to give one MEM forwarding for forwarding B.

 

Hazard 2

```
01c283b3  add x7 x5 x28
01c3f333  and x6 x7 x28
0003f313  andi x6 x7 0
400302b3  sub x5 x6 x0
0062d463  bge x5 x6 8 <right_branch>
```

instruction: 01c3f333 and x6 x7 x28

hazard type: data hazard on x7

resolve: give an EX forwarding on forwarding A

instruction: 0003f313 andi x6 x7 0

hazard type: data hazard on x7

resolve: give an MEM forwarding on forwarding A

instruction: 400302b3 sub x5 x6 x0

0062d463 bge x5 x6 8 <right_branch>


hazard type: data hazard on x6 and control hazard

resolve: give an EX forwarding on forwarding A for two clock cycles, and an MEM forwarding on forwarding B for one clock cycle, with forwarding_eq1=1 for one clock cycle, and use the hazard detection unit to add bubbles in it: PC_write=0, IFID_write=0, mux_con=0 for one clock cycle.

instruction: 0062d463 bge x5 x6 8 <right_branch>

hazard type: data hazard on x5

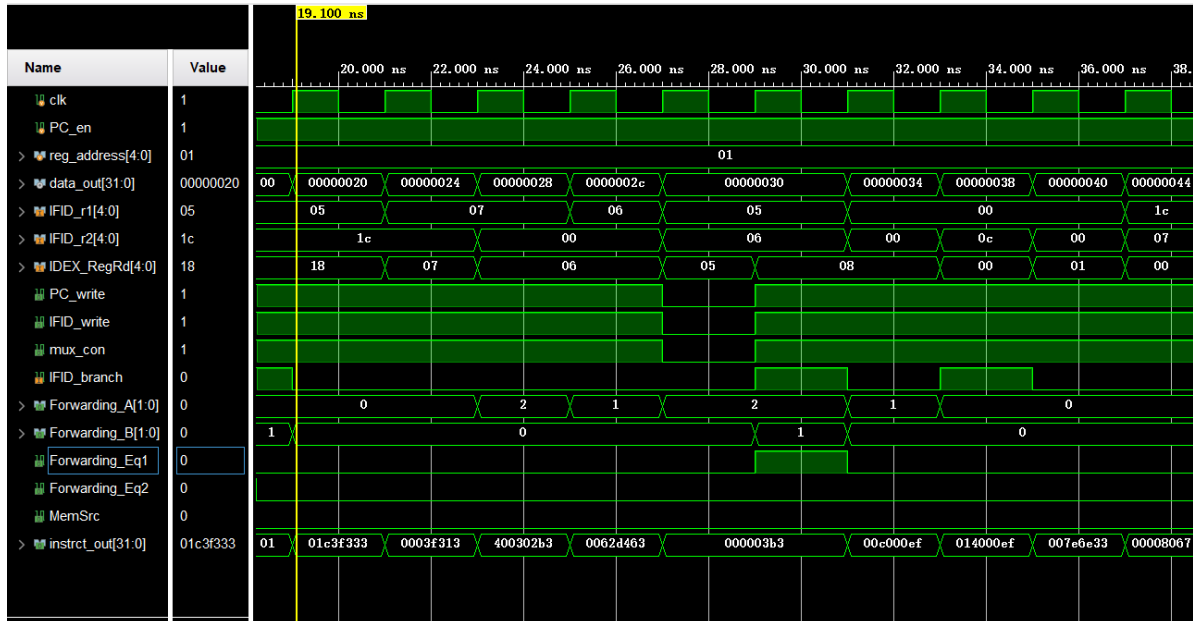resolve: give an MEM forwarding on forwarding A



RTL Design

